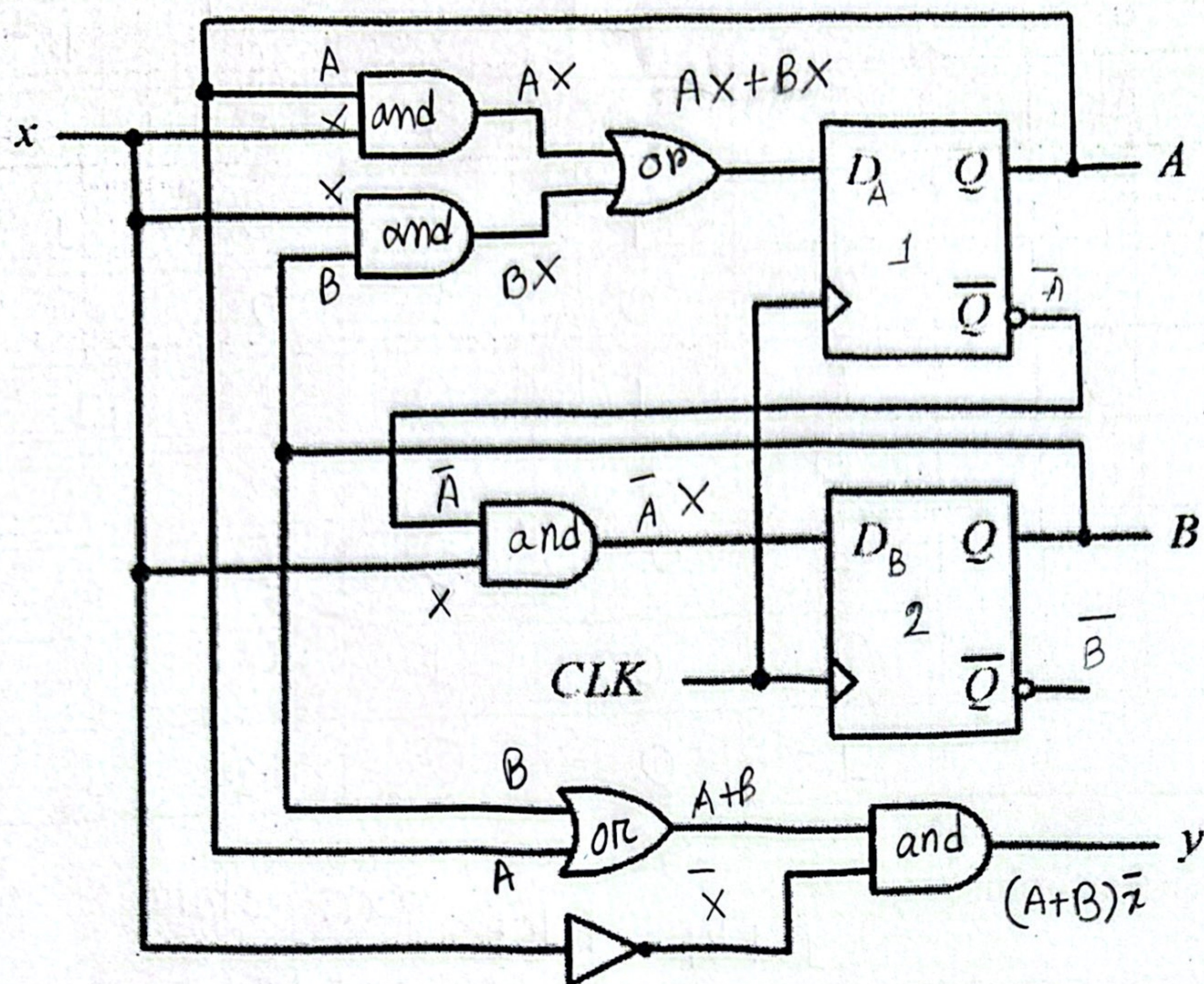


Draw the state diagram of the given circuit:



i. How many flip-flops are there? \Rightarrow

ii.

Present State(s)	A, B or $(A(t), B(t))$
Next State(s)	A^+, B^+ or $(A(t+1), B(t+1))$
Input(s)	D_A, D_B, x
Output(s)	y

iii. Equations:

D_A	$AX + BX$
D_B	$\bar{A}x$
y	$(A+B)\bar{x}$

iv + v.

A	B	x	Da	Db	y	A ⁺	B ⁺
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	0	0	1	0	0
0	1	1	1	1	0	1	1
1	0	0	0	0	1	0	0
1	0	1	1	0	0	1	0
1	1	0	0	0	1	0	0
1	1	1	1	0	0	1	1

D Flip-Flop Characteristic Table:

Q(t) [Present State]	D	Q(t + 1) [Next State]
0	0	0
0	1	1
1	0	0
1	1	1

vi. State Diagram: input output

